

Part A

Practical Exercise 2: Circuit Design

Part A

1. Circuit (a)

$$\text{voltage} = \text{current} \times \text{resistance}$$

$$\text{resistance} = 20 + 30 + 50 \\ = \underline{\underline{100\Omega}}$$

Circuit (b)

$$\text{voltage} = \text{current} \times \text{resistance}$$

$$\text{resistance} = \left(\frac{1}{20} + \frac{1}{100} + \frac{1}{50} \right)^{-1} \\ = \left(\frac{5 + 1 + 2}{100} \right)^{-1} \\ = \left(\frac{8}{100} \right)^{-1} \\ = 100/8 \\ = \underline{\underline{12.5\Omega}}$$

2. circuit (a)

$$\text{voltage} = \text{current} \times \text{resistance}$$

$$\text{current} = \frac{125}{100} \\ = \underline{\underline{1.25A}}$$

circuit (b)

$$\text{voltage} = \text{current} \times \text{resistance}$$

$$\text{current} = \frac{125}{12.5} \\ = \underline{\underline{10A}}$$

3. circuit (a)

- resistors in series
- current is equal
- current in all resistors = $\underline{\underline{1.25A}}$

circuit (b)

- resistors in parallel
- voltage is equal

$$\text{voltage} = \text{current} \times \text{resistance}$$

At 20Ω

$$\text{current} = \frac{125}{20} \\ = \underline{\underline{6.25A}}$$

At 100Ω

$$\text{current} = \frac{125}{100} \\ = \underline{\underline{1.25A}}$$

At 50Ω

$$\text{current} = \frac{125}{50} \\ = \underline{\underline{2.5A}}$$

4. circuit (a)

- resistors in series
- current is equal
- voltage = current $\times$ resistance

At 20Ω

$$\text{voltage} = 1.25 \times 20 \\ = \underline{\underline{25V}}$$

At 30Ω

$$\text{voltage} = 1.25 \times 30 \\ = \underline{\underline{37.5V}}$$

At 50Ω

$$\text{voltage} = 1.25 \times 50 \\ = \underline{\underline{62.5V}}$$

circuit (b)

- resistors in parallel
- voltage is equal
- voltage in each resistor = $\underline{\underline{125V}}$

5. circuit (a)

$$\text{power} = \text{voltage} \times \text{current}$$

At 20Ω

$$\text{power} = 25 \times 1.25 \\ = \underline{\underline{31.25W}}$$

At 30Ω

$$\text{power} = 37.5 \times 1.25 \\ = \underline{\underline{46.875W}}$$

circuit (b)

$$\text{power} = \text{voltage} \times \text{current}$$

At 20Ω


$$\text{power} = 125 \times 6.25 \\ = \underline{\underline{781.25W}}$$

At 100Ω

$$\text{power} = 125 \times 1.25 \\ = \underline{\underline{156.25W}}$$

Part B


Circuit Diagram 1

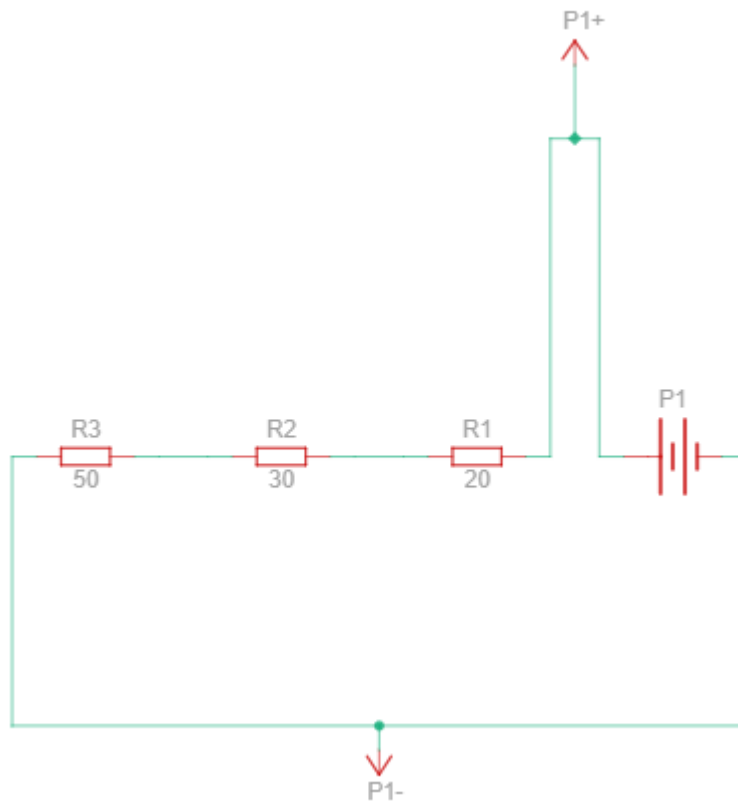

Component List

1. Power Supply (P1): 125V, 1.25A
2. Resistor (R3): 50Ω
3. Resistor (R2): 30Ω
4. Resistor (R1): 20Ω
5. Jumper wires: 4


Circuit Diagram 2

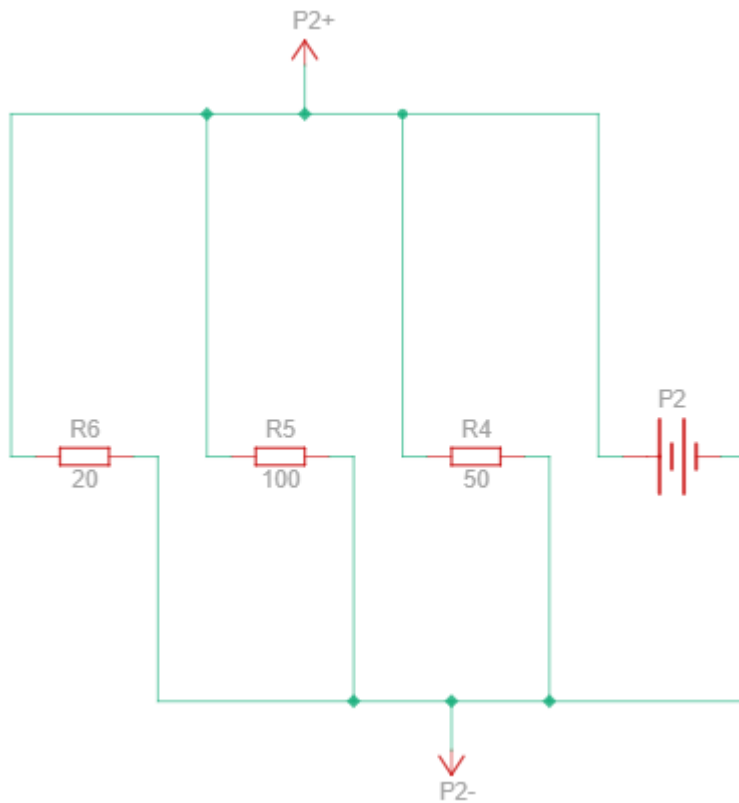

Component List

1. Power Supply (P2): 125V, 12.5A
2. Resistor (R6): 20Ω
3. Resistor (R5): 100Ω
4. Resistor (R4): 50Ω
5. Jumper wires: 6

Circuit Diagram 3

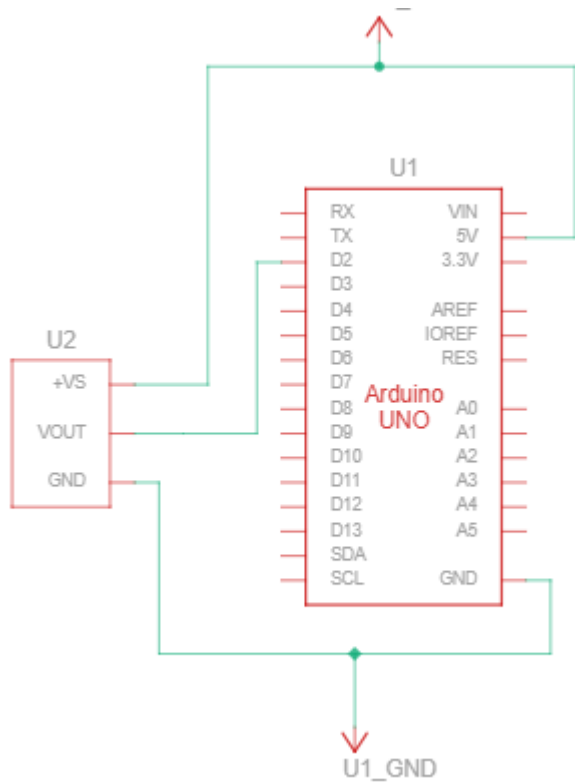

Component List

1. Arduino Uno (used in place of Arduino Nano since Tinkercad doesn't have Arduino Nano)
2. Breadboard (small)
3. Temperature Sensor
4. Jumper wires: 5